

Assignment 3

Instructions

- For this homework, you may only use:
 - a) All of the components under Wiring
 - b) All of the components under Gates **EXCEPT** for **Controlled Buffer**, **Controlled Inverter**, **PLA**
 - c) All of the components under Plexers
 - d) All of the components under Arithmetic
 - e) All of the components under Memory **EXCEPT** for **ROM**, and **Random Generator**
 - f) You can use in-built Logisim components like **Adder**, **Subtractor**, **MUX**, etc
- Please label all inputs and outputs.
- Please form groups of two for this assignment.
- Write down your and your teammate's names and OS used in the comment section of your Canvas submission.
- Download your `.circ` file once done and upload that file on Canvas.
- Assignment 3 will be a total of 100 points.
- Good luck!

You have been provided a Register File circuit in the starting circuit. The **only outputs** of the register file that you are allowed to use are `A_Out` and `B_Out`.

Starter file: (Download it first, then open it on Logisim)

Mac: [Link](#)

Windows: [Link](#)

CPU.circ (100 points)

Build a 16-bit single cycle CPU (with a 4-bit opcode) that can implement the given instructions.

Instruction Format

Our CPU will be using fixed length instructions. Our CPU will also have two types of instruction formats: R-type and I-type. In R-type instructions both operands come from registers. In I-type instructions, the first operand comes from a register and the second will be contained within the instruction.

R-Type

Name	Bits	Description
OpCode	15 - 12	Determines what operation should be performed
C	11 - 8	The destination register. The C in $\text{Reg}_C = \text{Reg}_A \text{ OP } \text{Reg}_B$
A	7 - 4	The first source register. The A in $\text{Reg}_C = \text{Reg}_A \text{ OP } \text{Reg}_B$
B	3 - 0	The second source register. The B in $\text{Reg}_C = \text{Reg}_A \text{ OP } \text{Reg}_B$

I-Type

Name	Bits	Description
OpCode	15 - 12	Determines what operation should be performed
C	11 - 8	The destination register. The C in $\text{Reg}_C = \text{Reg}_A \text{ OP } \text{Imm}$
A	7 - 4	The first source register. The A in $\text{Reg}_C = \text{Reg}_A \text{ OP } \text{Imm}$
Immediate	3 - 0	The second source register. The Imm in $\text{Reg}_C = \text{Reg}_A \text{ OP } \text{Imm}$

Instructions

Operation	Encoding (The value in the OpCodeField)	Description
NOPx	0000	Do nothing
STOP	0001	The CPU ceases execution
ADDRx	0010	$\text{Reg}_C = \text{Reg}_A + \text{Reg}_B$
SUBRx	0011	$\text{Reg}_C = \text{Reg}_A - \text{Reg}_B$

ANDRx	0100	$\text{Reg}_C = \text{Reg}_A \text{ AND } \text{Reg}_B$
ORRx	0101	$\text{Reg}_C = \text{Reg}_A \text{ OR } \text{Reg}_B$
XORRx	0110	$\text{Reg}_C = \text{Reg}_A \text{ XOR } \text{Reg}_B$
ADDIx	0111	$\text{Reg}_C = \text{Reg}_A + \text{Immediate}$
SUBIx	1000	$\text{Reg}_C = \text{Reg}_A - \text{Immediate}$
ANDIx	1001	$\text{Reg}_C = \text{Reg}_A \text{ AND } \text{Immediate}$
ORIx	1010	$\text{Reg}_C = \text{Reg}_A \text{ OR } \text{Immediate}$
XORI	1011	$\text{Reg}_C = \text{Reg}_A \text{ XOR } \text{Immediate}$
NEGATEx	1100	$\text{Reg}_C = -\text{Reg}_A$
NOTx	1101	$\text{Reg}_C = \text{NOT } \text{Reg}_A$
MOVEx	1110	$\text{Reg}_C = \text{Reg}_A$
LOADx	1111	$\text{Reg}_C = \text{Immediate}$

Inputs

Pin	Size (in bits)	Explanation
Instruction	16	The instruction located at Instruction_Address
ClkIn	1	The Clock. Connect this to the clock ports of your registers/flip-flops. Do nothing else with this.

Outputs

Pin	Size (in bits)	Explanation
Instruction_Address_Out	5	The address of the instruction you want to execute
Reg0-15	4	The values in the register file. This has already been connected for you

CPU Components

Your CPU should have

- A Program Counter (PC)
 - This stores and keeps track of what instruction you are on
 - Your PC will increment by 2 for each clock cycle.
- Instruction Decoder
 - This is a bunch of combinational logic that sets the control signals inside of your CPU
- Register File
 - A bunch of registers as well as ways to specify which ones you want. This has already been created for you.
 - The **only outputs** of the register file that you are allowed to use are A_Out and B_Out.

The Example Program

Instruction	Meaning	Result
LOAD REG ₀ , 3 x	Reg ₀ = 3	Reg ₀ = 3
LOAD REG ₁ , 6 x	Reg ₁ = 6	Reg ₁ = 6
NOPx	Do Nothing	No Change
MOVE REG ₂ , Reg1	Reg ₂ = Reg ₁	Reg ₂ = 6
ANDR REG ₃ , REG ₀ , REG ₁	REG ₃ = REG ₀ AND REG ₁	REG ₃ = 3 & 6 = 2
ANDI REG ₄ , REG ₃ , 3	REG ₄ = REG ₃ AND 3	REG ₄ = 2 & 3 = 2
ORR REG ₅ , Reg ₂ , REG ₀	REG ₅ = Reg ₂ OR REG ₀	REG ₅ = 6 3 = 7
ORI REG ₆ , Reg ₃ , 12	REG ₆ = Reg ₃ OR 12	REG ₆ = 2 OR 12 = 14
XORR REG ₇ , Reg ₂ , REG ₀ x	REG ₇ = Reg ₂ XOR REG ₀	REG ₇ = 6 ^ 3 = 5
XORI REG ₈ , Reg ₆ , 15	REG ₈ = Reg ₆ XOR 15	REG ₈ = 14 ^ 15 = 1
NEG REG ₉ , REG ₃	REG ₉ = -REG ₃	REG ₉ = -2
ADDR REG ₁₀ , Reg ₇ , REG ₇	REG ₁₀ = Reg ₇ + REG ₇	REG ₁₀ = 5 + 5 = 10

The test program is just an **example program**. Your CPU should function on **any program** given to it.